

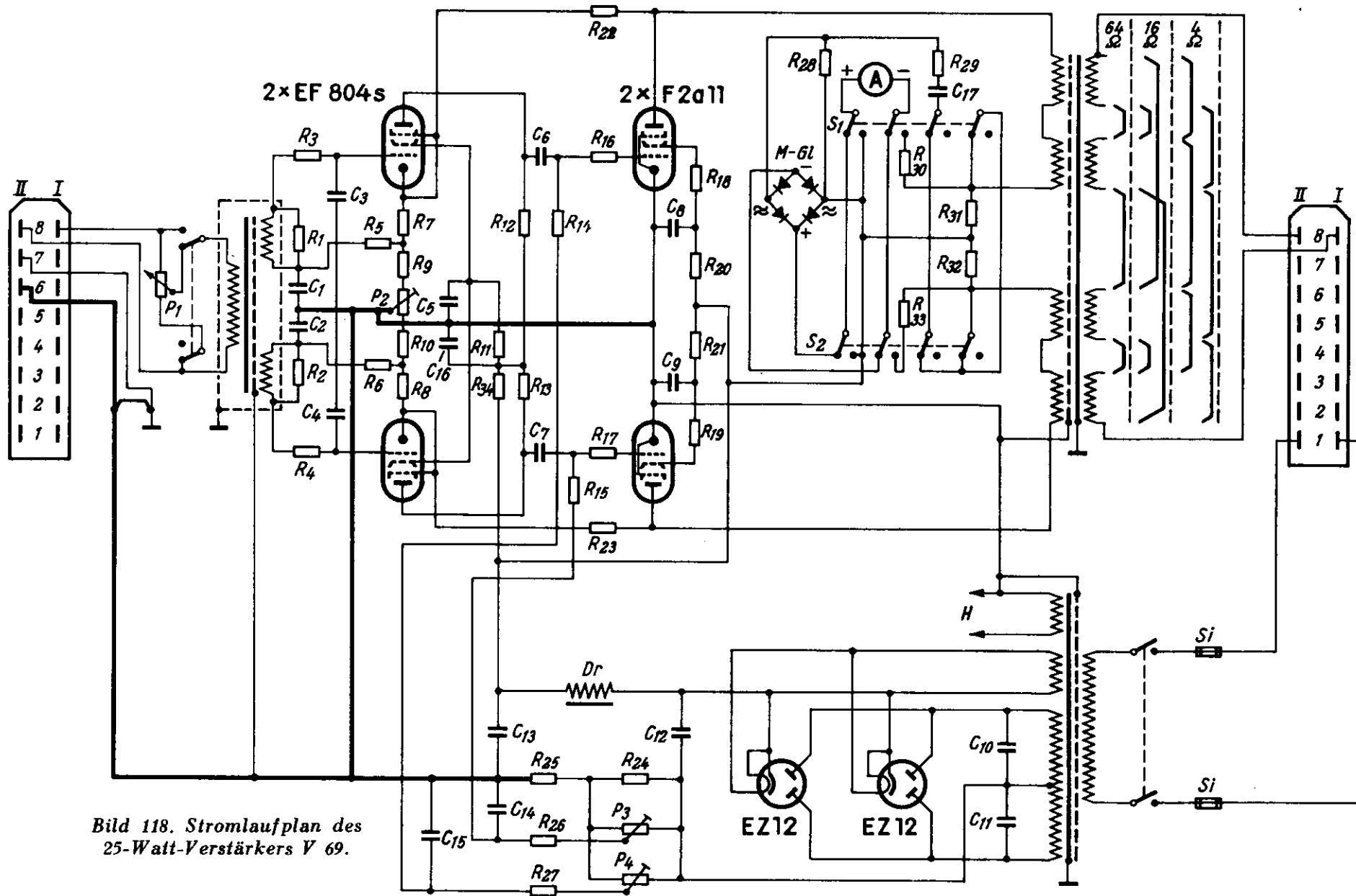


Bild 118. Stromlaufplan des
25-Watt-Verstärkers V 69.

$R_1 = 250\text{ k}\Omega$	$R_{11} = 1\text{ M}\Omega$	$R_{21} = 5\text{ k}\Omega$	$R_{31} = 30\text{ }\Omega$	$C_2 = 1\text{ }\mu\text{F}$	$C_{12} = 16\text{ }\mu\text{F}$
$R_2 = 250\text{ k}\Omega$	$R_{12} = 300\text{ k}\Omega$	$R_{22} = 100\text{ k}\Omega$	$R_{32} = 30\text{ }\Omega$	$C_3 = 10\text{ pF}$	$C_{13} = 16\text{ }\mu\text{F}$
$R_3 = 250\text{ k}\Omega$	$R_{13} = 300\text{ k}\Omega$	$R_{23} = 100\text{ k}\Omega$	$R_{33} = 28\text{ k}\Omega$	$C_4 = 10\text{ pF}$	$C_{14} = 1\text{ }\mu\text{F}$
$R_4 = 250\text{ k}\Omega$	$R_{14} = 300\text{ k}\Omega$	$R_{24} = 100\text{ }\Omega$	$R_{34} = 50\text{ k}\Omega$	$C_5 = 1\text{ nF}$	$C_{15} = 1\text{ }\mu\text{F}$
$R_5 = 500\text{ k}\Omega$	$R_{15} = 300\text{ k}\Omega$	$R_{25} = 50\text{ }\Omega$	$P_1 = 5\text{ k}\Omega$	$C_6 = 50\text{ nF}$	$C_{16} = 4\text{ }\mu\text{F}$
$R_6 = 500\text{ k}\Omega$	$R_{16} = 1\text{ k}\Omega$	$R_{26} = 10\text{ k}\Omega$	$P_2 = 1\text{ k}\Omega$	$C_7 = 50\text{ nF}$	$C_{17} = 0,1\text{ }\mu\text{F}$
$R_7 = 500\text{ }\Omega$	$R_{17} = 1\text{ k}\Omega$	$R_{27} = 10\text{ k}\Omega$	$P_3 = 5\text{ k}\Omega$	$C_8 = 1\text{ }\mu\text{F}$	
$R_8 = 500\text{ }\Omega$	$R_{18} = 100\text{ }\Omega$	$R_{28} = 10\text{ k}\Omega$	$P_4 = 5\text{ k}\Omega$	$C_9 = 1\text{ }\mu\text{F}$	
$R_9 = 900\text{ }\Omega$	$R_{19} = 100\text{ }\Omega$	$R_{29} = 6\text{ k}\Omega$		$C_{10} = 10\text{ nF}$	
$R_{10} = 900\text{ }\Omega$	$R_{20} = 5\text{ k}\Omega$	$R_{30} = 28\text{ k}\Omega$	$C_1 = 1\text{ }\mu\text{F}$	$C_{11} = 10\text{ nF}$	